



Faculty of Engineering and Technology  
Department of Electrical and Computer Engineering

ENCS 2110

**EXP 3 Post-Lab:** Encoders, Decoders, Multiplexers, and Demultiplexers


**Student's name:** Anas Al Sayed

**Student's No.:** 1221020

**Section:** 10

**Instructor:** Hanya Radwan

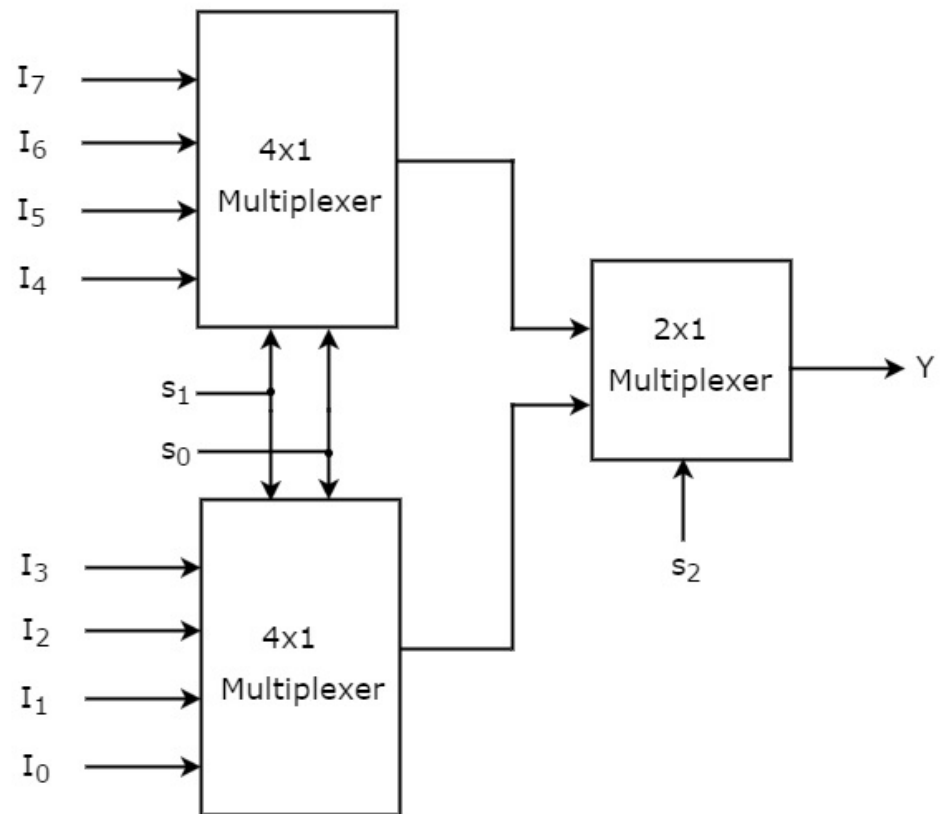✓ Implement 8x1 Multiplexer using lower order Multiplexers Show how to solve it.



✓ Design a Majority Circuit; a circuit that takes 4 inputs  $A, B, C, D$  and 1 output  $Y$ . Its output equals 1 when 3 or 4 of the inputs are 1. You can only use two 4x1 multiplexers.

